




## Laboratory Report #4

Name: Josh Ratificar Date Completed: 10-02-2023

Laboratory Exercise Title: Dataflow Modeling of Combinational Circuits

### Block Diagrams:

 

*Above includes the block diagrams for this Laboratory Exercise. Based on the diagrams, the following can be concluded:*

### 4-Bit Comparator

#### 8-Input Ports:

- A[0], A[1], A[2], A[3], B[0], B[1], B[2], B[3]

#### 3-Output Ports:

- R[2], R[1], R[0]

### NOTE

G (“greater than” is TRUE) | R [2] = G (1 if A > B, else 0)

E (“equal to” is TRUE) | R [1] = E (1 if A = B, else 0)

L (“less than” is TRUE) | R [0] = L (1 if A < B, else 0)


## Exercise 4A:

```

1  /*****
2  *   FILE:           FourBitComparator.v
3  *   AUTHOR:        Josh Ratificar
4  *   Class:         Gr.3 CpE 3101L Introduction to HDL
5  *   Group/Schedule Friday, 7:30 AM to 10:30 AM
6  *   Description:   FourBitComparator.v module
7  *****/
8  module FourBitComparator(
9      input  [3:0]A,
10     input  [3:0]B,
11     output [2:0]R
12 );
13     wire [2:0]common;
14     // A > B @ R[2] | R[2] = G (1 if A > B, else 0)
15     assign R[2] = (A > B)? 1'b1 : 1'b0;
16
17
18     // A = B @ R[1] | R[1] = E (1 if A = B, else 0)
19     assign R[1] = (A == B)? 1'b1 : 1'b0;
20
21     // A < B @ R[0] | R[0] = E (1 if A < B, else 0)
22     assign R[0] = (A < B)? 1'b1 : 1'b0;
23 endmodule
24

```

**Figure 1.0 – FourBitComparator.v Script**

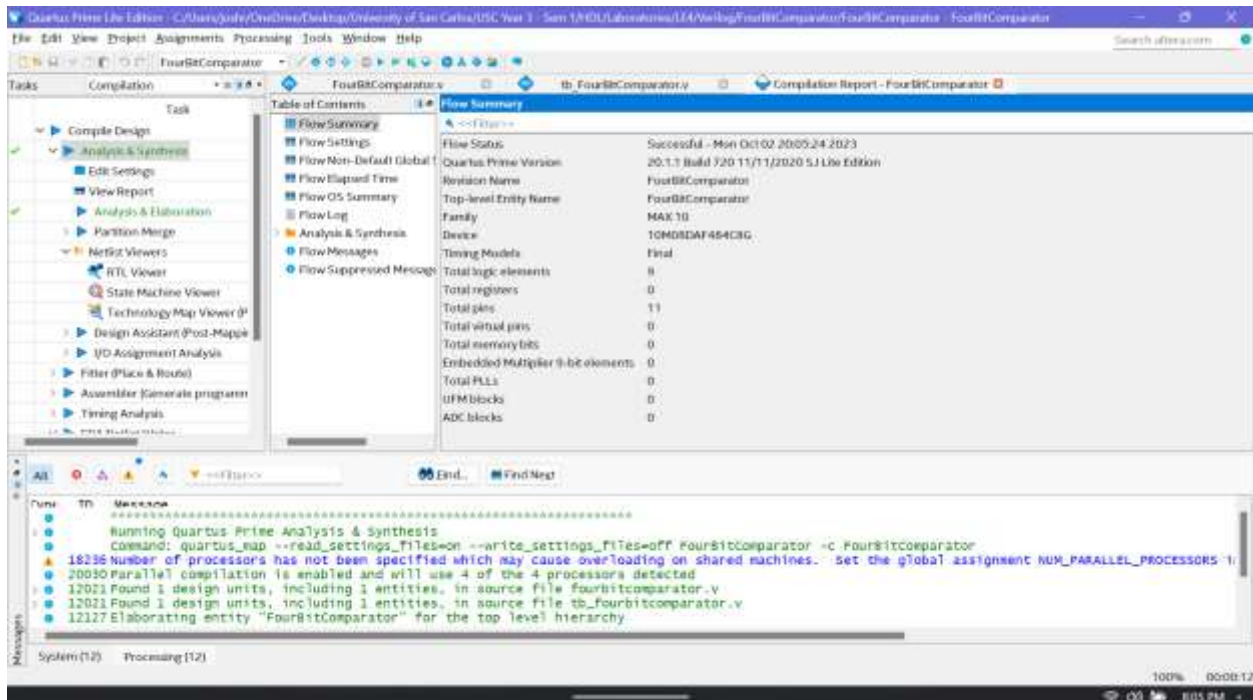

**Figure 1.1 – FourBitComparator.v Analysis and Elaboration Test Results**

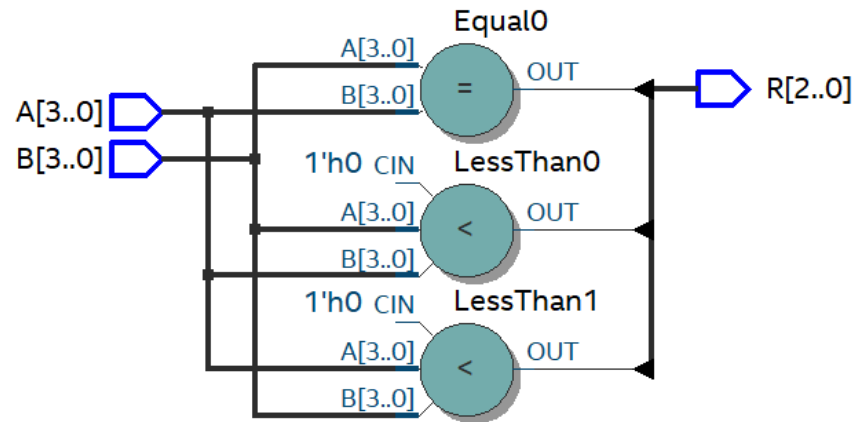



Figure 1.2 – FourBitComparator RTL View Output

```

1  /*****
2  *   FILE:                tb_FourBitComparator.v
3  *   AUTHOR:              Josh Ratificar
4  *   CLASS:               Gr.3 CpE 3101L Introduction to HDL
5  *   Group/Schedule       Friday, 7:30 AM to 10:30 AM
6  *   Description:         tb_FourBitComparator.v module
7  *****/
8  `timescale 1 ns / 1 ps
9  module tb_FourBitComparator();
10     reg [3:0] A, B;
11     wire [2:0] R;
12     FourBitComparator UUT(
13         .A(A),
14         .B(B),
15         .R(R)
16     );
17     initial begin
18         $display("Test Bench | tb_FourBitComparator...");
19         // Test cases for A < B
20         $display("A < B");
21         A = 4'b0100; B = 4'b1010; #10; // A < B
22         A = 4'b1100; B = 4'b1111; #10; // A < B
23         A = 4'b0010; B = 4'b1101; #10; // A < B
24         A = 4'b0011; B = 4'b1101; #10; // A < B
25
26         // Test cases for A = B
27         $display("A = B");
28         A = 4'b1110; B = 4'b1110; #10; // A = B
29         A = 4'b1111; B = 4'b1111; #10; // A = B
30         A = 4'b1000; B = 4'b1000; #10; // A = B
31         A = 4'b0000; B = 4'b0000; #10; // A = B
32
33         // Test cases for A > B
34         $display("A > B");
35         A = 4'b0001; B = 4'b0000; #10; // A > B
36         A = 4'b1111; B = 4'b1110; #10; // A > B
37         A = 4'b0101; B = 4'b0011; #10; // A > B
38         A = 4'b0010; B = 4'b0001; #10; // A > B
39         $stop;
40     end
41     initial begin
42         $monitor("Time = %2d ns\t A = %d | [%b]\t B = %d [%b]\t R = %b", $time, A, A, B, B, R);
43     end
44 endmodule
45

```

Figure 1.3 – tb\_FourBitComparator.v Script for Testing Module

 

**Figure 1.4 – Four Bit Comparator RTL Simulation Output**

```
# Test Bench | tb_FourBitComparator...
# A < B
# Time = 0 ns A = 4 | [0100] B = 10 [1010] R = 001
# Time = 10 ns A = 12 | [1100] B = 15 [1111] R = 001
# Time = 20 ns A = 2 | [0010] B = 13 [1101] R = 001
# Time = 30 ns A = 3 | [0011] B = 13 [1101] R = 001
# A = B
# Time = 40 ns A = 14 | [1110] B = 14 [1110] R = 010
# Time = 50 ns A = 15 | [1111] B = 15 [1111] R = 010
# Time = 60 ns A = 8 | [1000] B = 8 [1000] R = 010
# Time = 70 ns A = 0 | [0000] B = 0 [0000] R = 010
# A > B
# Time = 80 ns A = 1 | [0001] B = 0 [0000] R = 100
# Time = 90 ns A = 15 | [1111] B = 14 [1110] R = 100
# Time = 100 ns A = 5 | [0101] B = 3 [0011] R = 100
# Time = 110 ns A = 2 | [0010] B = 1 [0001] R = 100
# ** Note: $stop : C:/Users/joahnz/OneDrive/Desktop/University of San Carlos/USC Year 3 - Sem 1/HDL/Laboratories/LE4/Verilog/FourBitComparator/tb_FourBitComparator.v(39)
# Time: 120 ns Iteration: 0 Instance: /tb_FourBitComparator
# Break in Module tb_FourBitComparator at C:/Users/joahnz/OneDrive/Desktop/University of San Carlos/USC Year 3 - Sem 1/HDL/Laboratories/LE4/Verilog/FourBitComparator/tb_FourBitComparator.v line 39
V$IM2>
```

**Figure 1.5 – Four Bit Comparator Test Bench Monitor Output (Annotations to Figure 1.4)**

### Discussion of Results (Exercise 3A)

By observing the Test bench script (**Figure 1.3**), we expect that the respective R bit reflect the comparison between two four-bit inputs. This is the best-case desired behaviour expected which after simulating through RTL simulation (**Figure 1.4**), R appropriately and respectively changes every 40 ns. This is how the test bench was setup, and we can furthermore observe this behaviour in **Figure 1.5**. In conclusion, our design for our comparator works even when we applied Data Flow design in HDL Verilog.